



EEUC201 · ANALOG AND DIGITAL ELECTRONICS

Flip-Flops, Timers and Counters

S-R · D · T · J-K Flip-Flops — Clocked Design — Registers — Asynchronous & Synchronous Counters

Sequential logic building blocks: memory elements, storage registers, and binary counting circuits

Agenda



Basic Flip-Flops

S-R, D, T, and J-K flip-flop operation & truth tables

01



Clocked Flip-Flop Design

Excitation tables and the sequential design procedure

02



Registers

Shift register configurations for data storage & transfer

03



Asynchronous Counters

Ripple counters built from cascaded flip-flops

04



Synchronous Counters

Common-clock counters with parallel state transitions

05

What Is a Flip-Flop?

- A bistable memory element that stores one bit of binary data (0 or 1).
- Unlike a latch, a flip-flop changes state only in response to a clock edge (edge-triggered), not a level.
- Built from cross-coupled logic gates (NAND/NOR) forming a feedback loop with two stable outputs, Q and Q'.
- Four standard types: S-R, D, T, and J-K — each differs in how inputs control the next state.

LATCH vs FLIP-FLOP



Level-sensitive — output follows input while the enable is active.



Edge-triggered — output changes only at the rising or falling edge of the clock pulse.

Why it matters:

Edge-triggering prevents race conditions in multi-stage circuits, allowing predictable, synchronized data transfer between registers.

S-R Flip-Flop



Set-Reset Latch

- The simplest flip-flop: two inputs, S (Set) and R (Reset).
- $S = 1, R = 0 \rightarrow Q$ sets to 1
- $S = 0, R = 1 \rightarrow Q$ resets to 0
- $S = 0, R = 0 \rightarrow Q$ holds its previous state
- $S = 1, R = 1 \rightarrow$ Invalid / forbidden state (both outputs forced to same level)

Characteristic equation:

$$Q(\text{next}) = S + R' \cdot Q \quad (\text{with } S \cdot R = 0 \text{ constraint})$$

CHARACTERISTIC TABLE

S	R	Q(next)	Comment
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set

NAND-GATE IMPLEMENTATION



D Flip-Flop



Data / Delay Flip-Flop


- Has a single data input, D, plus a clock input.
- At the active clock edge, the output Q simply takes on the value present at D.
- Eliminates the invalid state problem of the S-R flip-flop — D is never allowed to be both 1 and 0.
- Effectively delays the input by one clock period, hence the name 'Delay' flip-flop.
- Widely used in registers, memory cells, and pipeline stages.

CHARACTERISTIC TABLE

D	Q(next)
0	0
1	1

Characteristic equation: $Q(\text{next}) = D$

TIMING BEHAVIOUR

 

T Flip-Flop



Toggle Flip-Flop

- Has a single input, T (Toggle), plus a clock input.
- $T = 0 \rightarrow$ output holds its previous state.
- $T = 1 \rightarrow$ output toggles (complements) on every active clock edge.
- Often derived from a J-K flip-flop by tying J and K together ($J = K = T$).
- Ideal building block for binary counters, since successive bits toggle at half the frequency of the previous stage.

CHARACTERISTIC TABLE

T	Q(next)	Comment
0	Q	Hold
1	Q'	Toggle

Characteristic equation: $Q(\text{next}) = T \oplus Q$

FREQUENCY DIVISION ($T = 1$)



J-K Flip-Flop



The Universal Flip-Flop

- Improves on the S-R flip-flop by resolving the invalid input combination.
- $J = 0, K = 0 \rightarrow$ Hold (no change)
- $J = 0, K = 1 \rightarrow$ Reset ($Q = 0$)
- $J = 1, K = 0 \rightarrow$ Set ($Q = 1$)
- $J = 1, K = 1 \rightarrow$ Toggle (Q complements) — the previously forbidden case now has a defined, useful result.
- Called 'universal' because D, T, and S-R behaviour can all be derived from it.

CHARACTERISTIC TABLE

J	K	Q(next)	Comment
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set

$$Q(\text{next}) = J \cdot Q' + K' \cdot Q$$



No invalid state exists — every one of the four input combinations produces a well-defined, useful next state.


Four Types at a Glance

Type	Inputs	Characteristic Eqn.	Invalid State?	Typical Use
S-R	S, R	$Q(\text{next}) = S + R'Q$	Yes ($S=R=1$)	Basic latch, debounce
D	D	$Q(\text{next}) = D$	None	Registers, memory cells
T	T	$Q(\text{next}) = T \oplus Q$	None	Binary counters



D and T flip-flops can each be built from a J-K flip-flop: tie $J = D$, $K = D'$ for a D-type; tie $J = K = T$ for a T-type.

Clocked Flip-Flop Design Procedure

 

EXCITATION TABLES (INPUTS NEEDED FOR A GIVEN TRANSITION)

S-R

Q	Q(next)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

J-K

Q	Q(next)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

D

Q	Q(next)	D
0	0	0
0	1	1
1	0	0
1	1	1

T

Q	Q(next)	T
0	0	0
0	1	1
1	0	1
1	1	0

'X' denotes a don't-care condition — either input value produces the required transition, simplifying the resulting K-map.

Shift Registers

- A register is a group of flip-flops (typically D-type) used to store multiple bits of data.
- A shift register additionally moves stored bits left or right on each clock pulse — used for serial-to-parallel conversion, delay lines, and arithmetic operations.



Serial-In, Serial-Out



Data enters and exits one bit at a time — used purely as a time delay line.



Serial-In, Parallel-Out



Data loaded serially, then all bits read out simultaneously — common in UART receivers.



Parallel-In, Serial-Out



All bits loaded at once, then shifted out one at a time — used in UART transmitters.



Parallel-In, Parallel-Out



Bits loaded and read out simultaneously — acts as a simple buffer register.


Asynchronous (Ripple) Counters



Ripple-Clocked Design

- Only the first flip-flop is driven by the external clock; each subsequent flip-flop is clocked by the Q output of the previous stage.
- Built from T (or J-K wired as T) flip-flops toggling on every input pulse.
- The change 'ripples' through the chain — each flip-flop toggles slightly after the one before it, so delays accumulate stage by stage.
- n flip-flops divide the input frequency by 2^n and count from 0 to $2^n - 1$.
- Simple to build, but slower — not suitable for high-speed applications.

3-BIT RIPPLE COUNTER ($\div 8$)

 

Each stage toggles at half the frequency of the one before it


Synchronous Counters



Common-Clock Design

- Every flip-flop shares the same clock signal, so all outputs change at the same instant.
- Combinational logic (AND gates or J-K input equations) determines each flip-flop's next-state inputs from the current count.
- No cumulative ripple delay — total propagation delay equals that of a single flip-flop, regardless of counter length.
- Requires more design effort and gates than asynchronous counters, but supports much higher clock speeds.
- Preferred in high-speed digital systems and FPGA/ASIC designs.

3-BIT SYNCHRONOUS COUNTER

 

Common CLK (drives all stages simultaneously)

$$T1 = Q0 \quad T2 = Q0 \cdot Q1$$

(AND-gated feedback sets each T input)

All three flip-flops change state on the same clock edge — zero ripple delay.

Asynchronous vs Synchronous Counters

Aspect	Asynchronous (Ripple)	Synchronous
Clock connection	Only first FF gets external clock	All FFs share the same clock
Speed	Slower — delays accumulate stage by stage	Faster — single flip-flop delay only
Design complexity	Simple, minimal extra logic	More complex, needs combinational logic
Output glitches	Possible during transitions (ripple)	Clean, simultaneous transitions
Typical use	Low-speed, simple counting tasks	High-speed digital systems

SUMMARY

Key Takeaways



Flip-Flop Types

S-R (simple, has invalid state), D (delay), T (toggle), and J-K (universal, no invalid state)



Clocked Design

State diagram → state table → excitation table → K-maps → logic diagram



Registers

SISO, SIPO, PISO, and PIPO shift registers store and move multi-bit data



Counters

Asynchronous counters ripple and accumulate delay; synchronous counters share one clock for speed